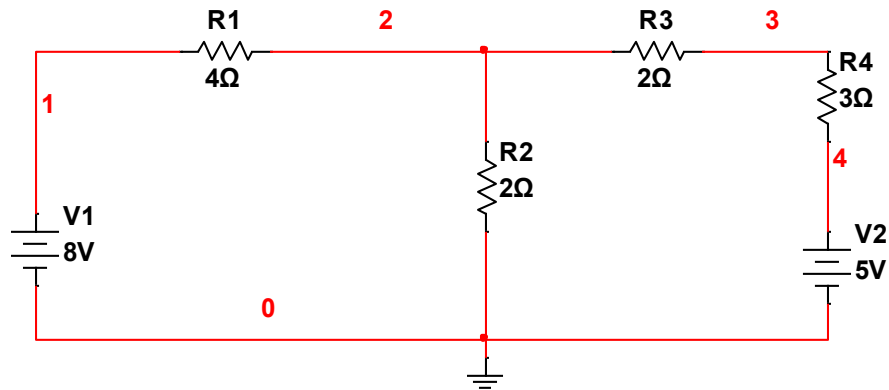



ET 252/L Lab 1

Perla Dominguez

Introduction: Simulating a two loop DC circuit to confirm handwritten circuit analysis results.



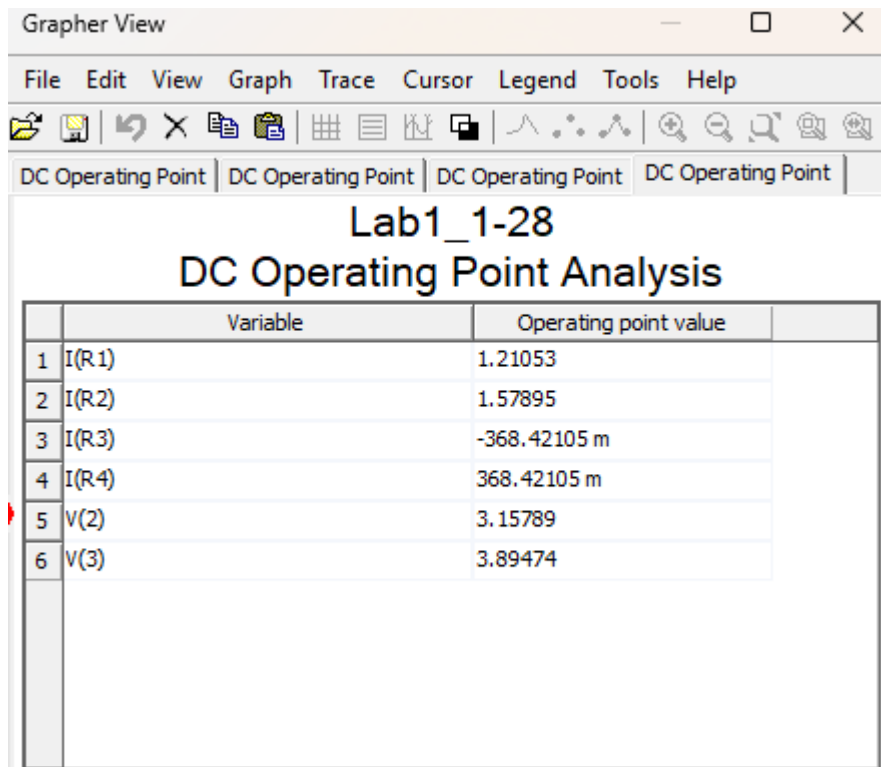Results: Simulation for DC operating point



ET 252/ Lab 2


Perla Dominguez

2/2/2026



Instruction: Modeled Nodal analysis on Multisim, as well as confirming voltage values in MatLab. Some values appear negative due to Multisim environment.

Nodal Analysis Schematic

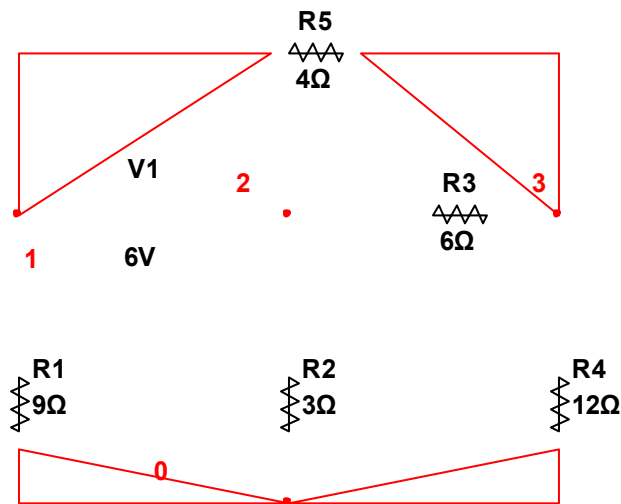

Simulation Results From Table


Design1		
DC Operating Point Analysis		
	Variable	Operating point value
1	V(1)	-4.21622
2	V(2)	1.78378
3	V(3)	-1.51351
4	I(R1)	-468.46847 m
5	I(R4)	-126.12613 m
6	I(R5)	-675.67568 m

ET 252 LAB 3

Perla Dominguez, [REDACTED]

Objective: We modeled a two mesh schematic on Multisim to verify voltage and current values through the nodes and branches. In this example, we wrote KCLs on paper to solve for V2. V1 was given, and V3 was hand calculated as well. This Multisim simulation proves that our math was correct on paper.

Schematic:

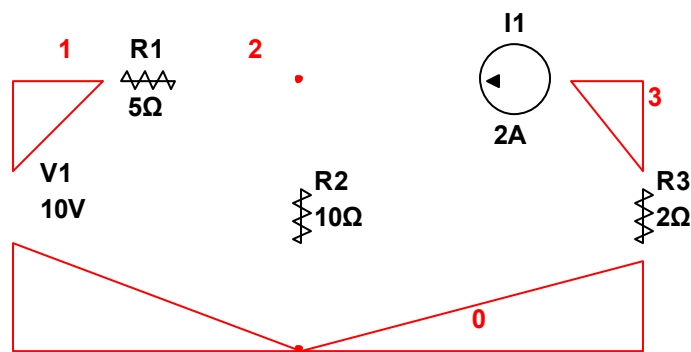

DC Operating Port Analysis Table:

Design1			
DC Operating Point Analysis			
	Variable	Operating point value	
1	V(1)	10.00000	
2	V(2)	13.33333	
3	V(3)	-4.00000	
4	I(R1)	-666.66667 m	
5	I(R2)	1.33333	
6	I(R3)	-2.00000	


ET 252: Lab 4

Perla Dominguez


2/4/2026

Instruction: Using Multisim to simulate three mesh circuit and to find voltage across each node, labeled as V1, V2, V3, in this example. In addition, we also test for current across each node modeling a virtual simulation of handwritten calculations.


Three Mesh Schematic Simulation:

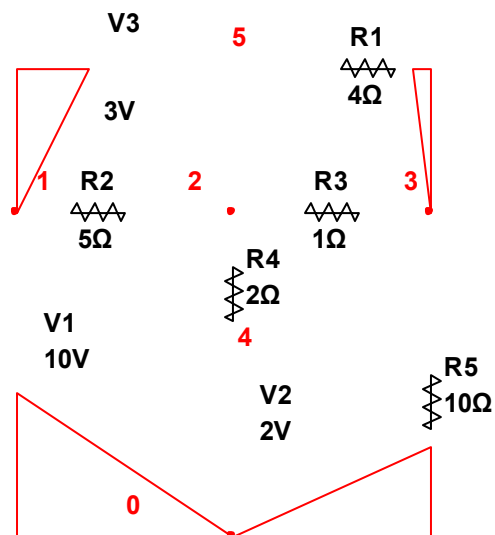

Resistor Values R1 – R5:

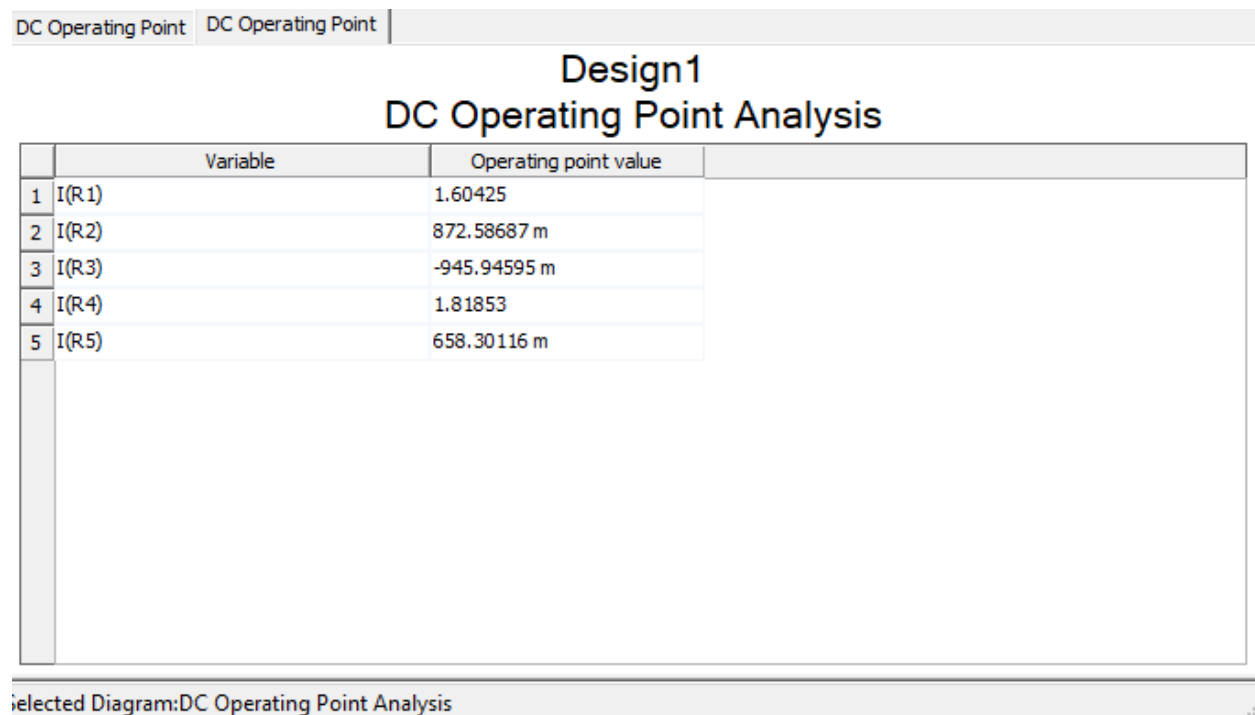

Voltage Across Nodes Simulation:

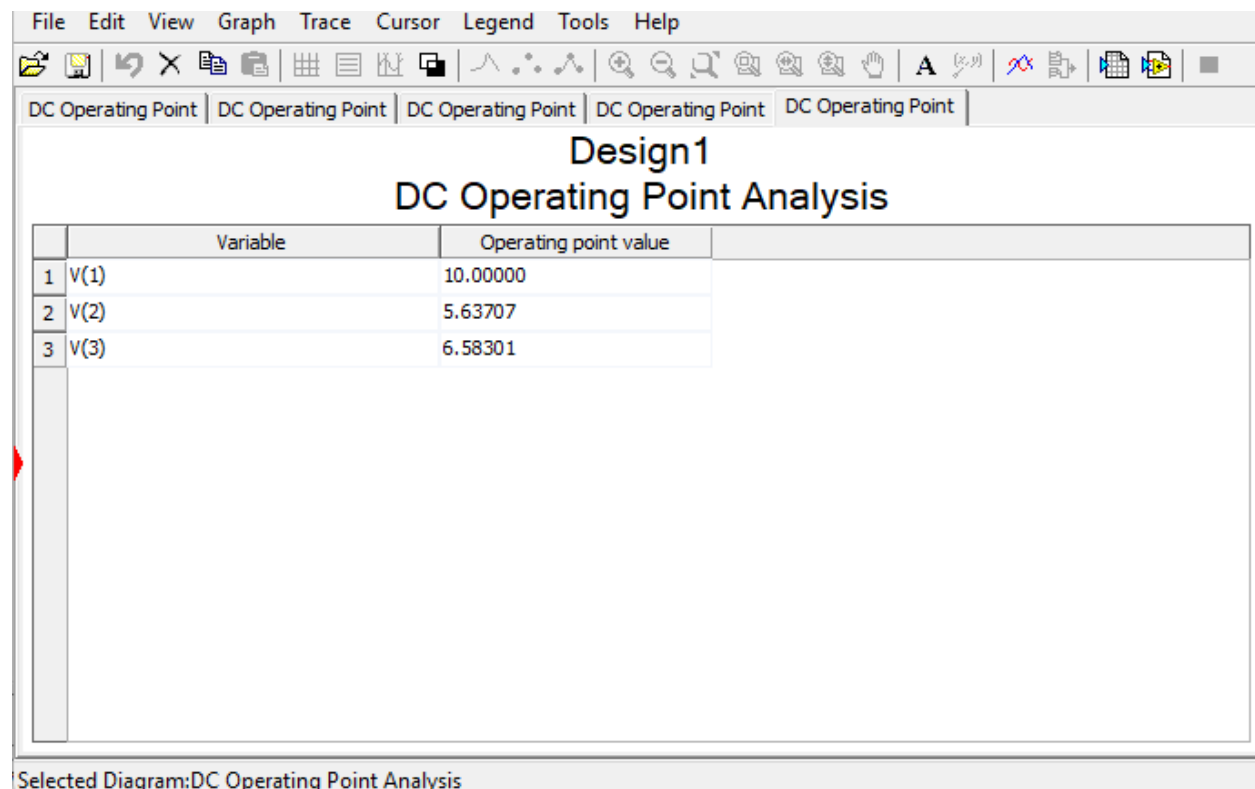


Perla Dominguez

2/25/2026


Lab 5

Objective: Using mutism, we modeled three different simulations to demonstrate a capacitor charging and displaying a waveform in seconds. We used three different kinds of transient graphs.


Schematic:

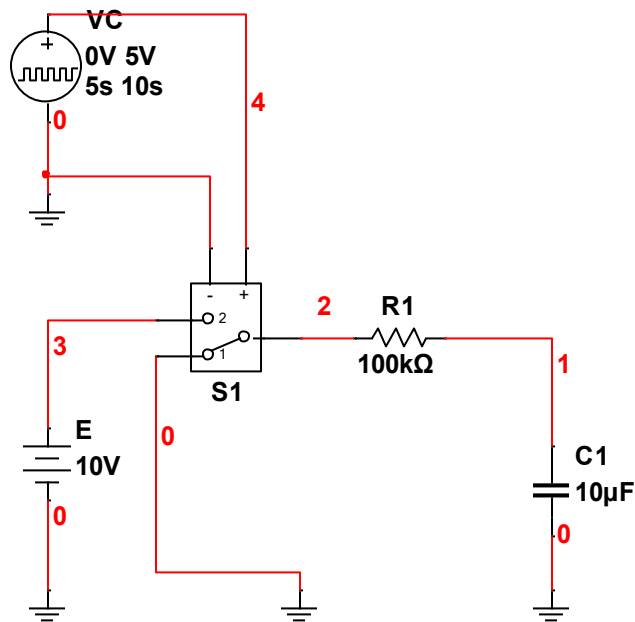


Square Waveform at Node 4:

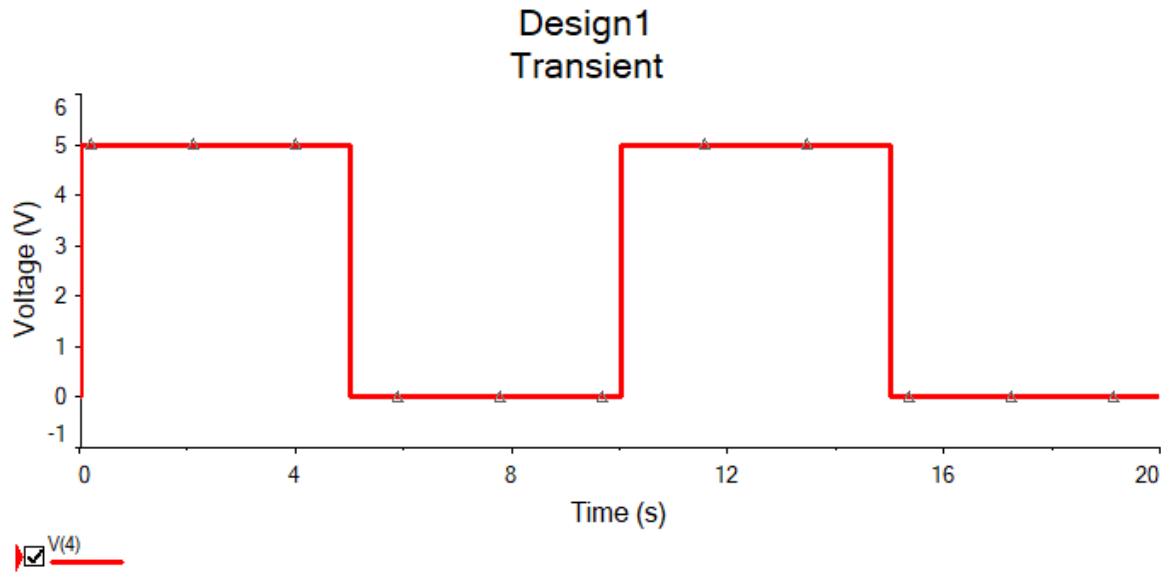

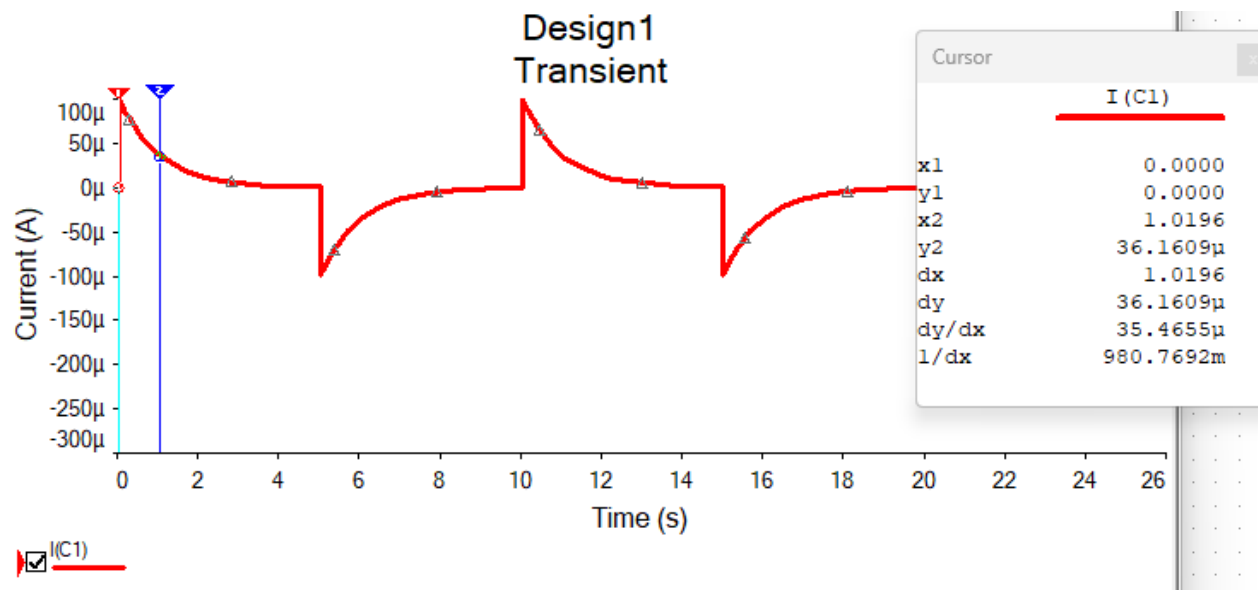Transient Simulation: Capacitor Charging and Discharging Current



Transient Simulation: Capacitor Voltage

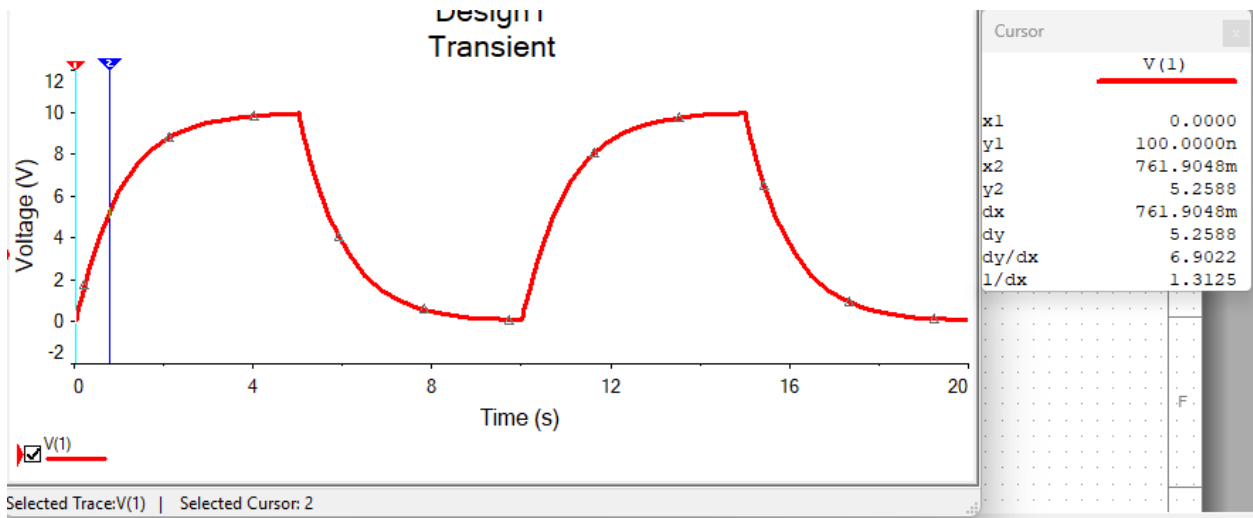

LAB EXPIREMENT 6


Perla Dominguez

ET 252 : CIRCUITS II


3/4/2026

Objective: In this lab, we focused on the transient response of an RC circuit, specifically observing the charging and discharging phases of a 10 microfarad capacitor. The circuit was powered by a 10 volt DC source and utilized two switches, S1 and S2, to control the flow of current through a 50 kilohm charging resistor and a 20 kilohm discharging resistor. As shown in the simulation results, closing S1 at 0.5 seconds initiated a charging phase where the capacitor voltage rose toward 10 volts, characterized by an initial current spike of approximately 100 microamps. Conversely, closing S2 at 5.0 seconds triggered a rapid discharge through the second resistor, resulting in a sharp negative current spike of approximately negative 500 microamps as the stored energy was released to ground.


Schematic:

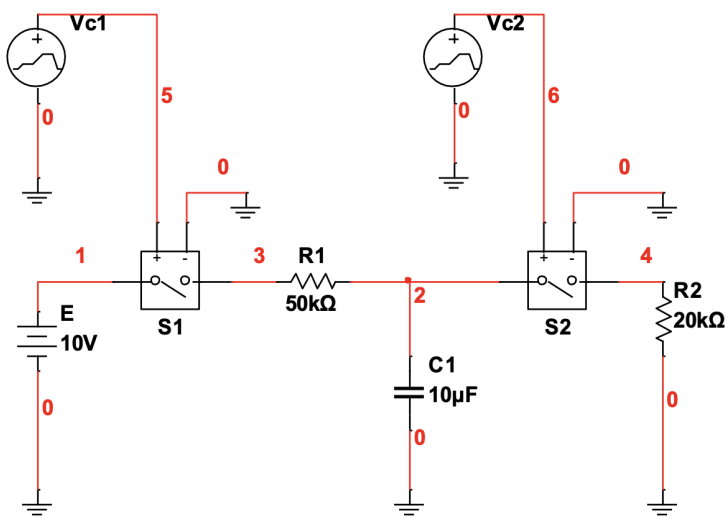


Transient Simulation 1:

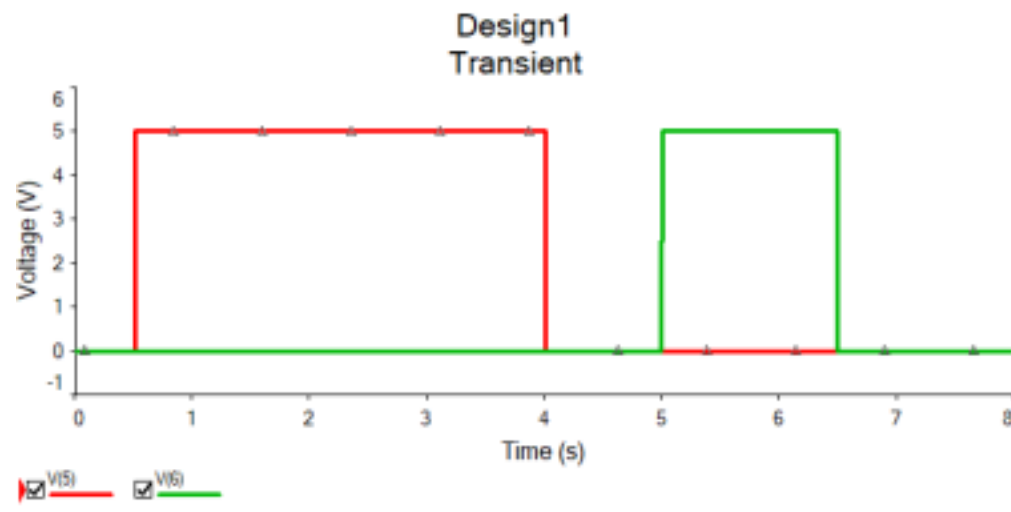

Transient Simulation 2:

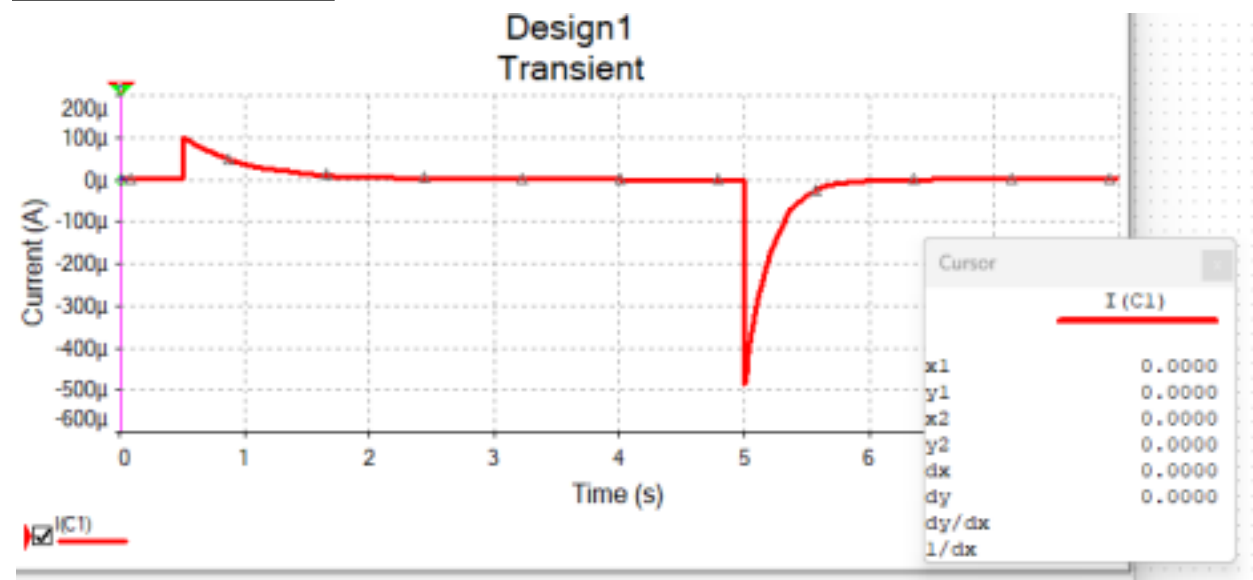

Transient Simulation 3:

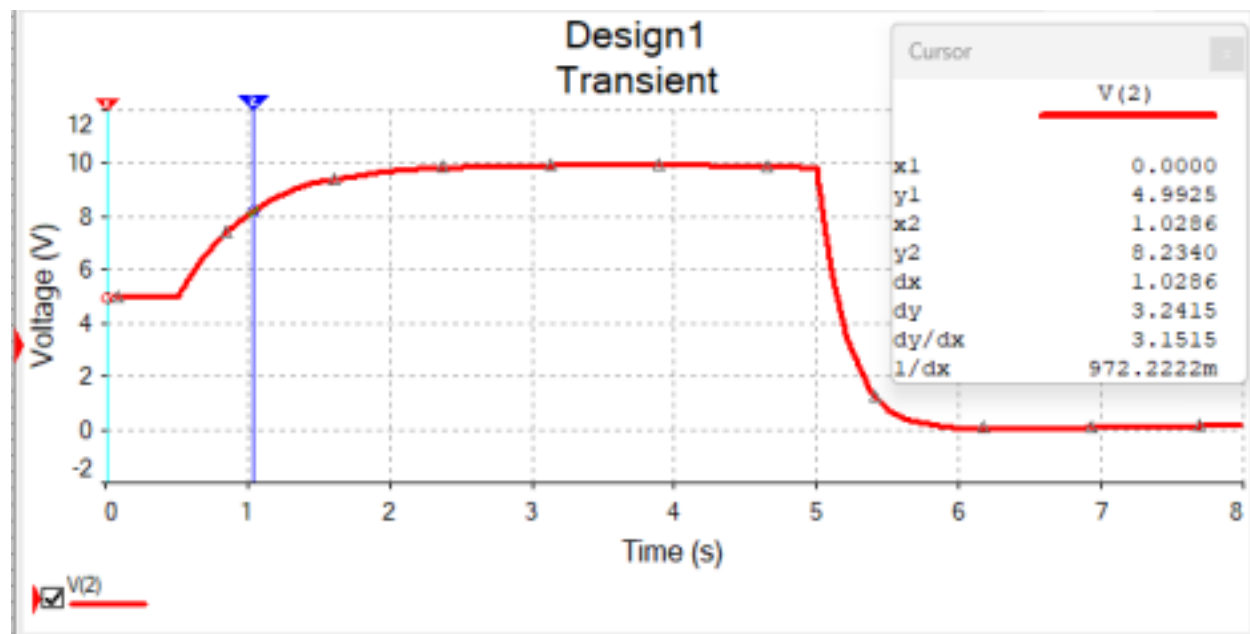

Perla Dominguez


ET 252/L


4/15/2026

Lab Experiment 7

Objective: In this lab experiment, we used a signal voltage source to model a parallel circuit to simulate steady-state behavior using sinusoidal excitation. The goal is to analyze the relationship between voltage and the combined current of resistive and capacitive branches in an AC environment

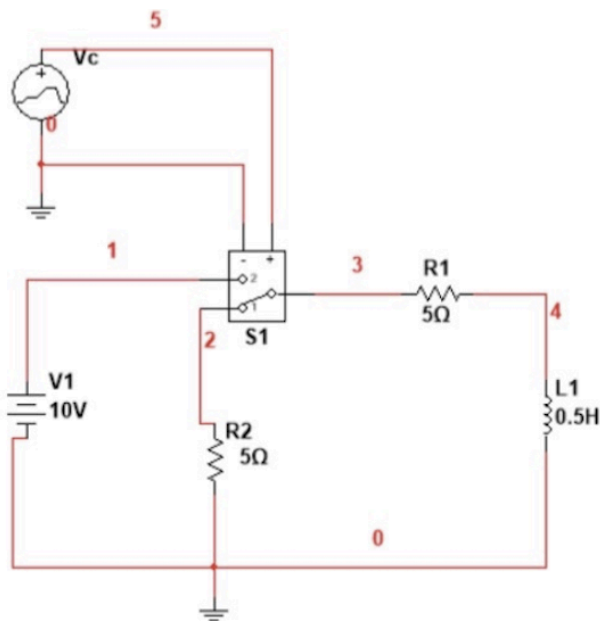Schematic: In this lab experiment, we have modeled an RL circuit. We modeled using a transient simulation to verify the storage and decay time constraints. We also verified voltage and current for our indicator.



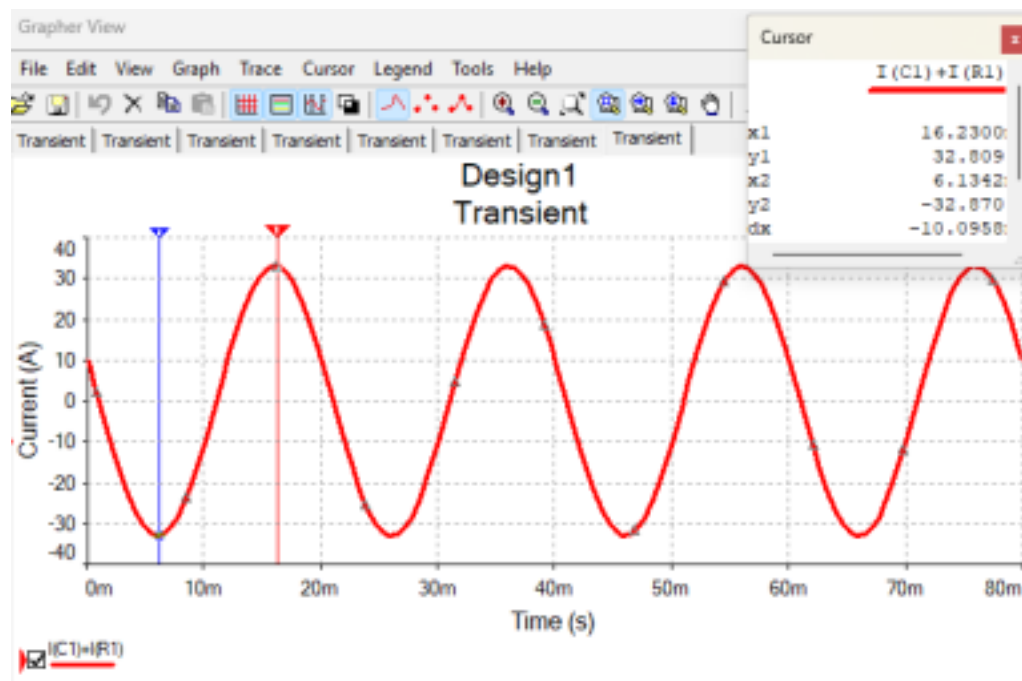

Perla Dominguez


3/23/2026

ET 252


Lab 8

Objective: In this lab, we proved the in class example shown in the circuit below by modeling it on Multisim. We captured four simulations, two of them being the inductor behavior and the other two capturing the resistor behavior. Overall this lab was informative in visualizing the behavior at these scenarios.


Schematic:

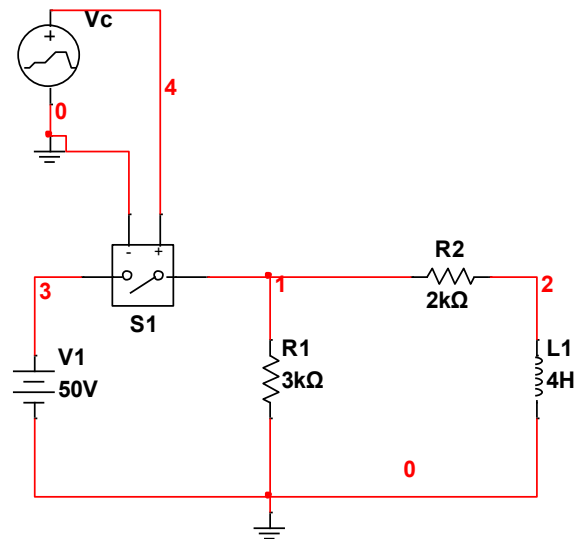


Simulation 1: VR2

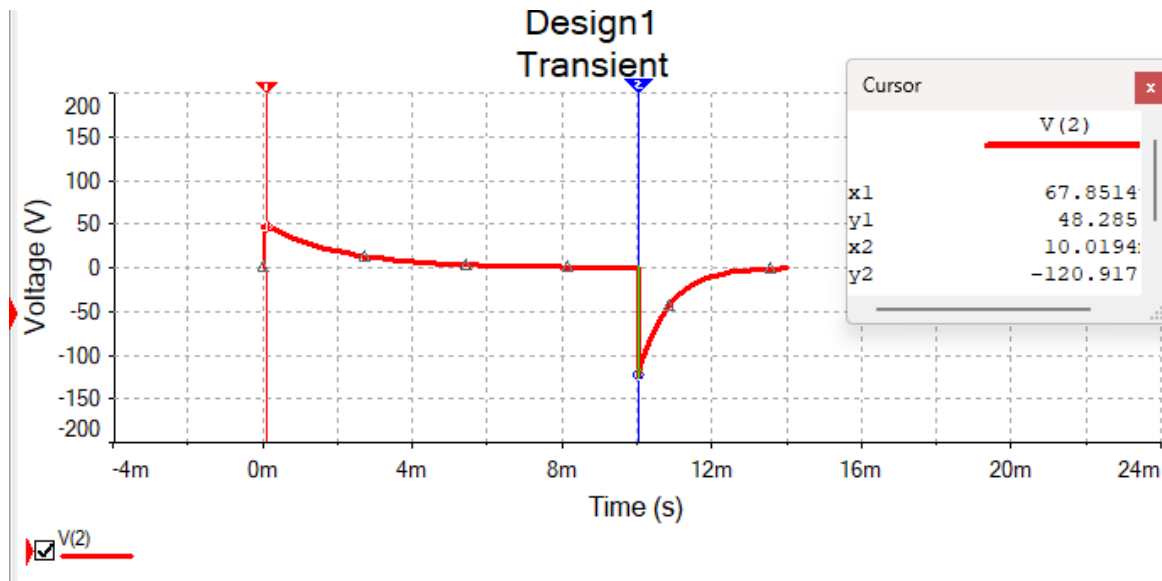


Simulation 2: VR1

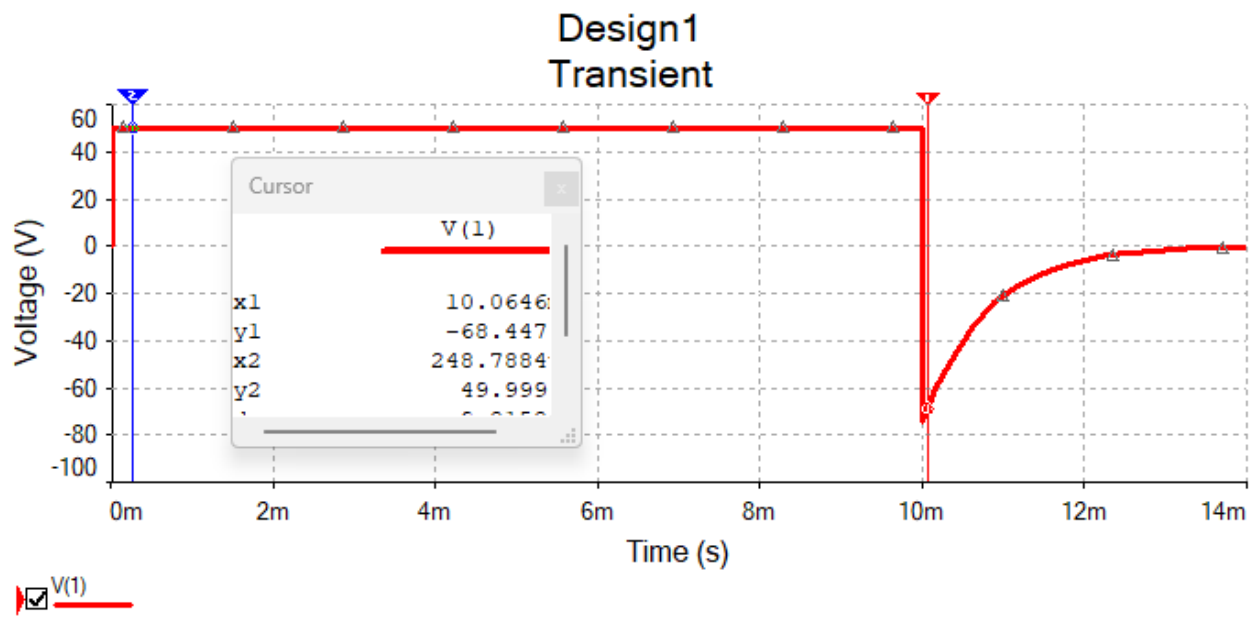

Simulation 3: Inductor Current

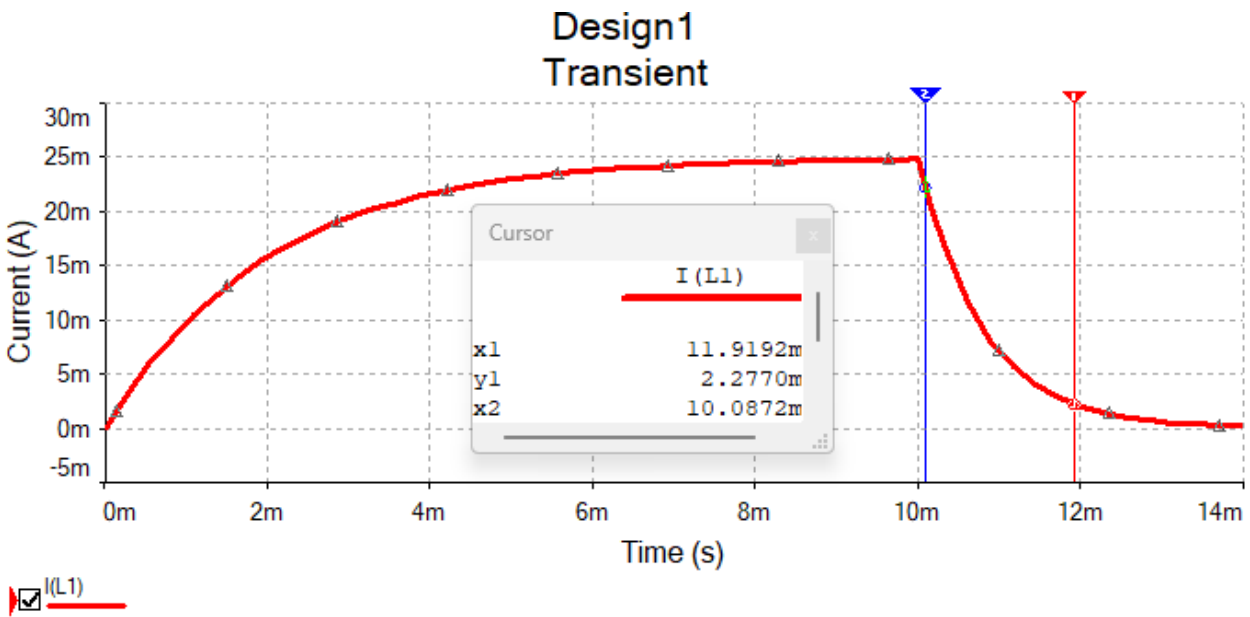

Simulation 4: Inductor Resistance

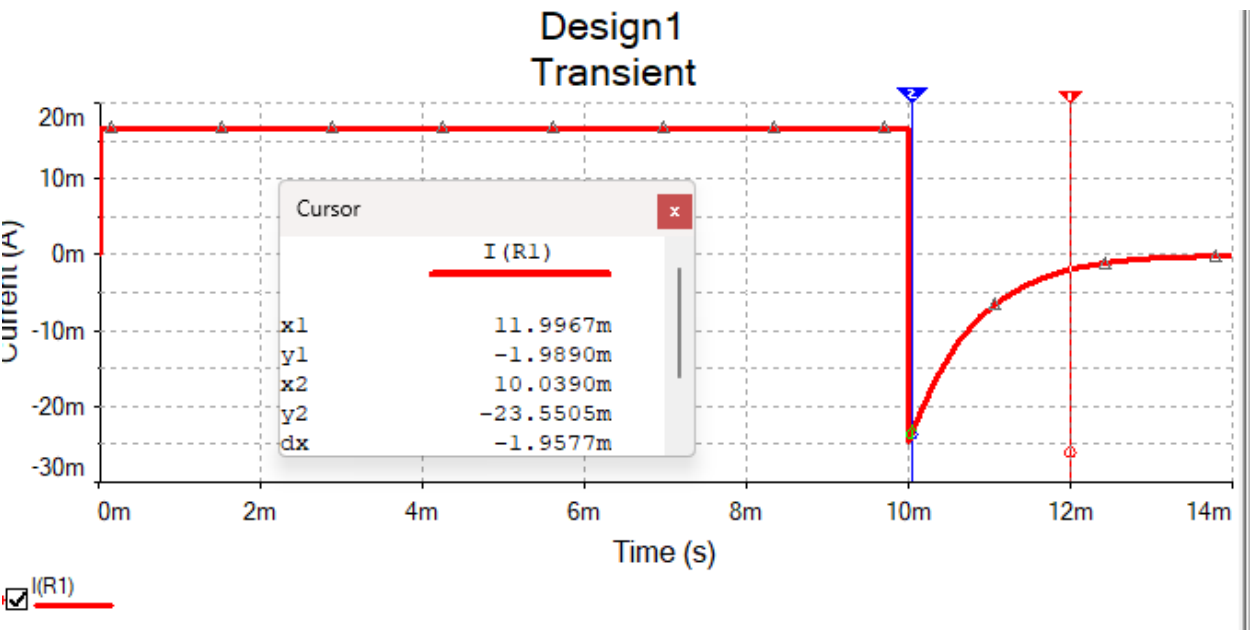

Perla Dominguez


ET 252/L


4/15/2026

Lab Experiment 9

Objective: In this lab experiment, we used a signal voltage source to model a parallel circuit to simulate steady-state behavior using sinusoidal excitation. The goal is to analyze the relationship between voltage and the combined current of resistive and capacitive branches in an AC environment

Schematic:

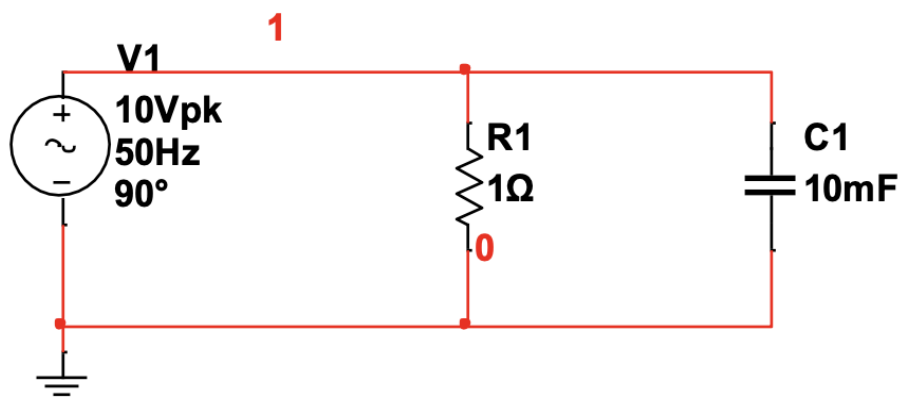

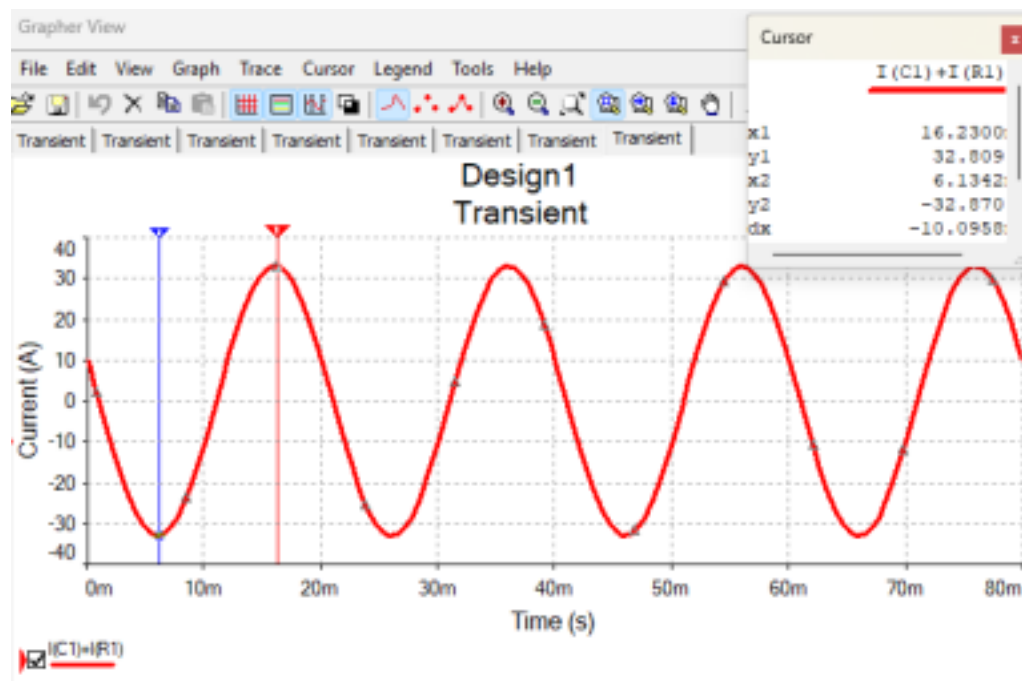

Perla Dominguez


ET 252

4/22/26

LAB 10



Objective: We analyzed an RLC circuit and verified calculations on multisim by using transient simulations.

Schematic:

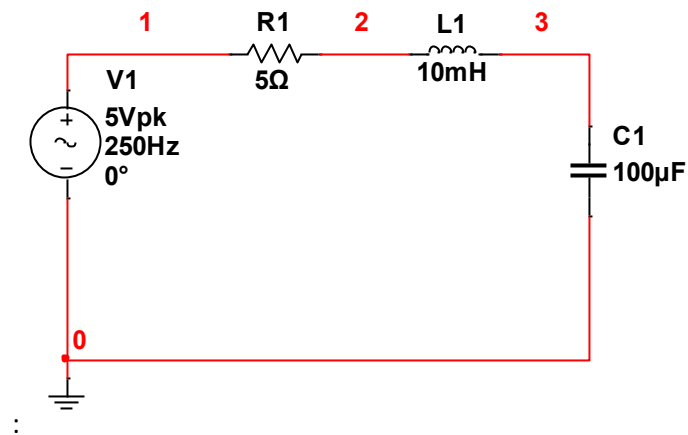

1. Compute admittance of RC parallel combination
$$x_L = 2\pi(250)(10 \times 10^{-3}) = 15.71 \text{ ohm}$$
$$x_C = 1 / 2\pi(250)(100 \times 10^{-6}) = 6.37 \text{ ohm}$$
$$x_1 = 15.71 - 6.37 = 9.34$$
2. Magnitude and Phase Angle
Magnitude: $\sqrt{5^2 + 9.34^2} = 10.60 \text{ ohm}$
Phase Angle: $\tan^{-1}(9.34/5) = 61.8 \text{ deg}$
3. Measured Peak
$$I_p = 5/10.60 = 0.47 \text{ A}$$
4. $(725.21 \times 10^{-6} / 0.004) \times 360 \text{ deg} = 65.27 \text{ deg}$

Transient Simulations:

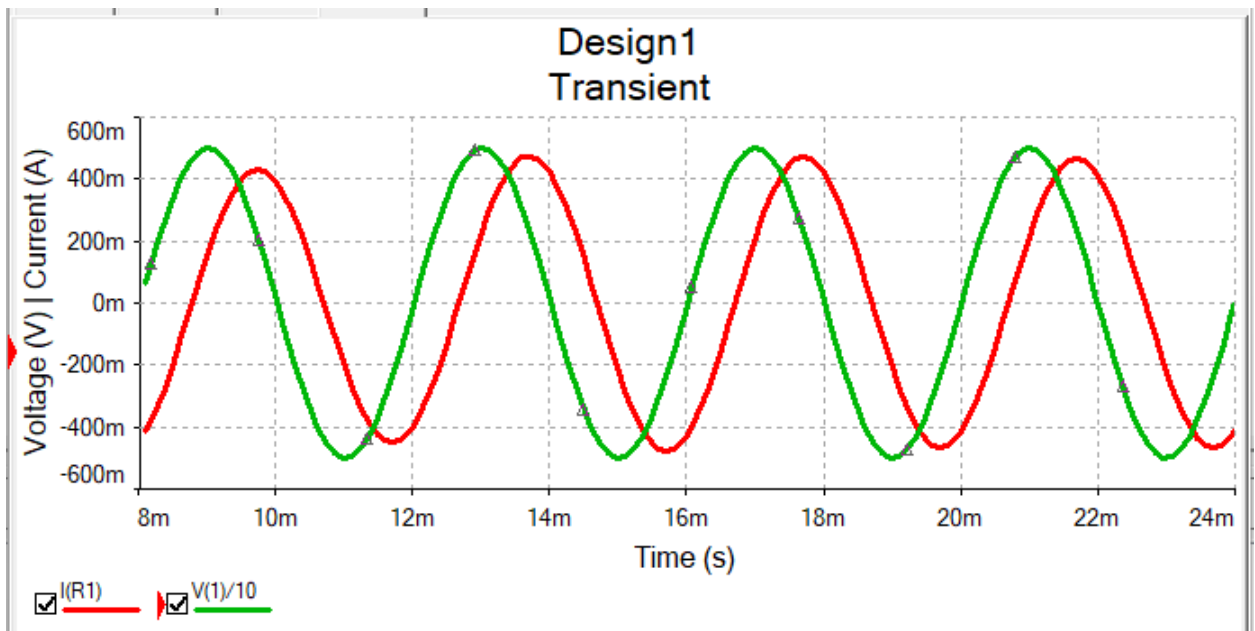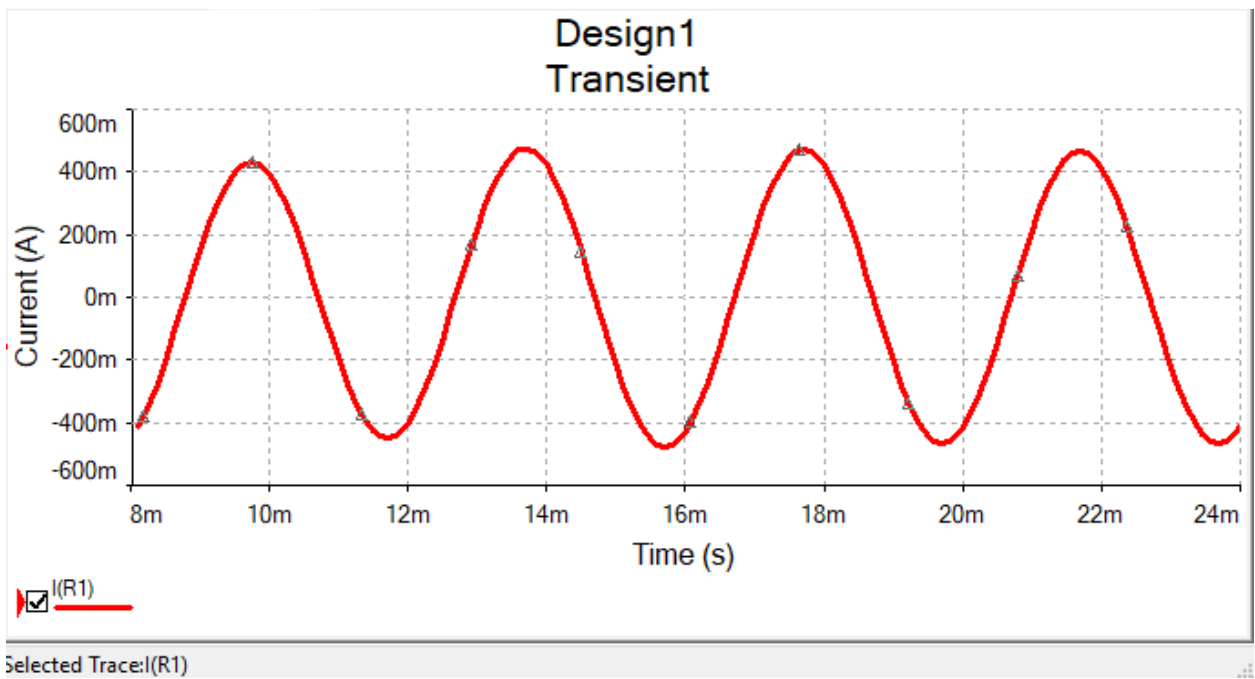

Perla Dominguez

5/4/2026



ET 252/L

Lab 11

Objective: This lab was broken down into two parts. On PART 1, we set up a notch filter on Multisim. This filter eliminates any frequency that is not desirable. This was achieved using an AC Sweep Simulation. We also calculated resonance frequency of parallel inductor and capacitor by hand and checked it with the software. In PART 2, we modeled an RLC Series low pass filter with a range. This was modeled using a sweep type Decade, 100 points per decade, and vertical scale decibel.

Part 1: Filter 1



Schematic:

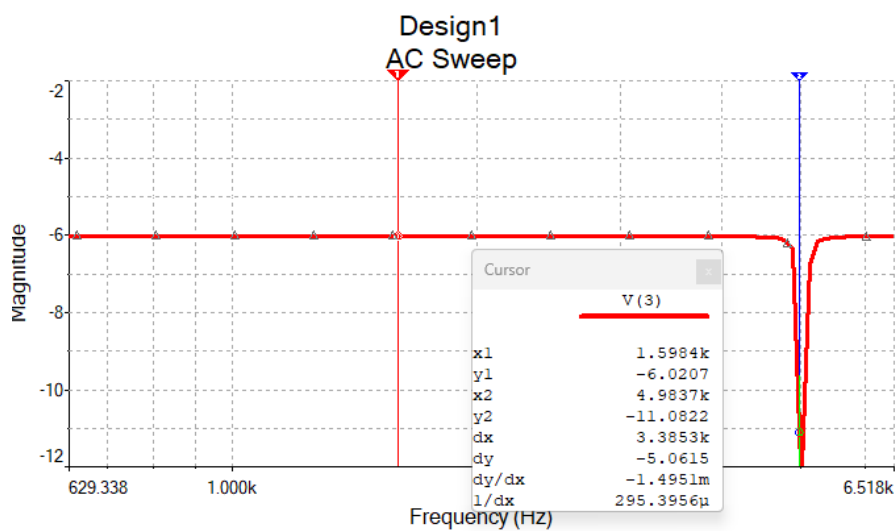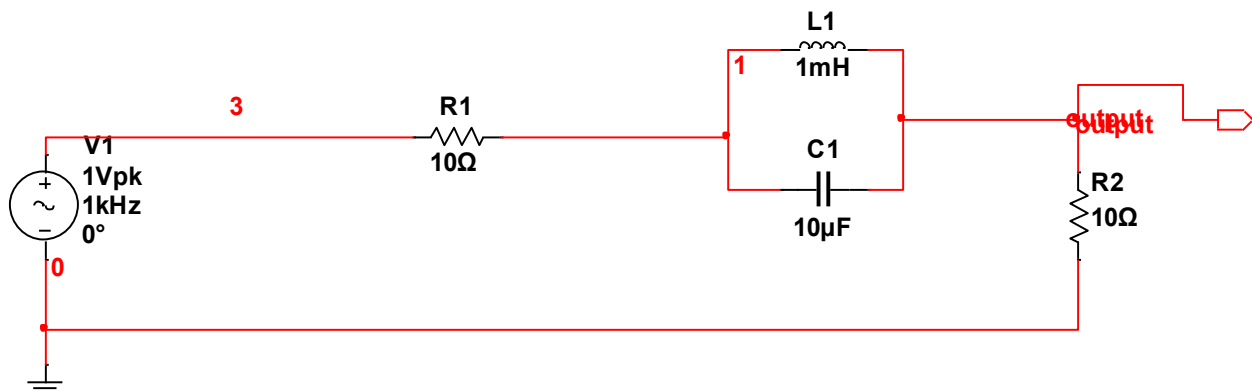

Resonant Frequency: $f(0) = 1.59\text{kHz}$

Part 2: Filter 2

Schematic:

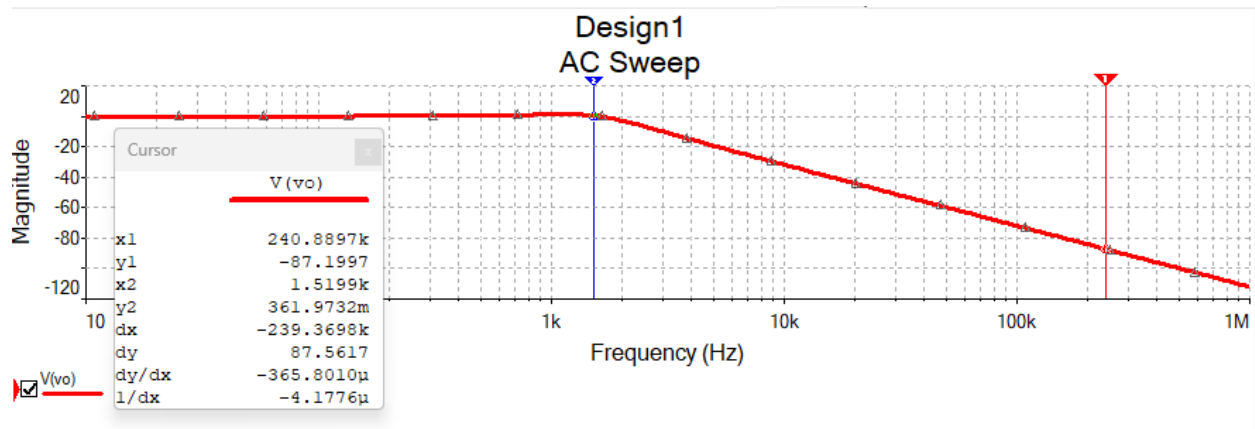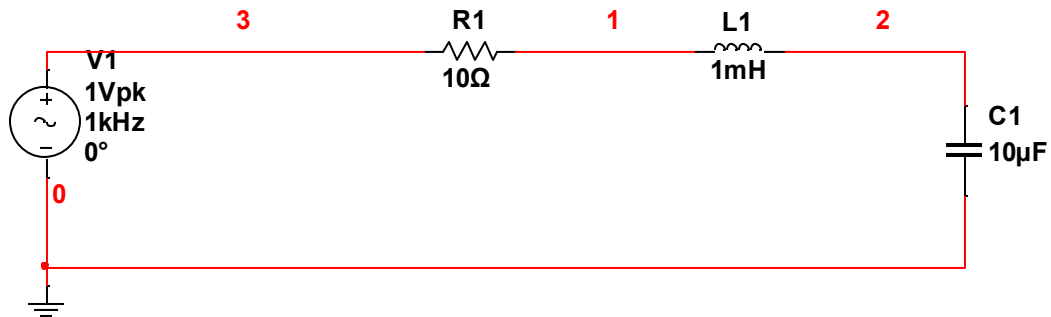

$$X1 = 240.99$$